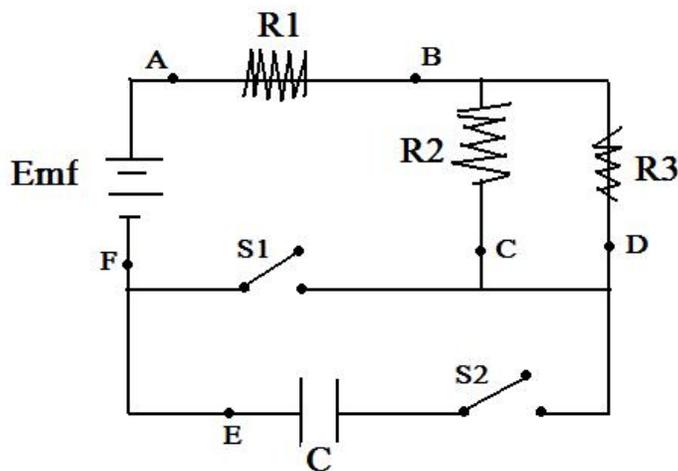


Measuring Along The (Conducting) Path From Pole to Pole

PHYSICS 204, YAVERBAUM

JOHN JAY COLLEGE OF CRIMINAL JUSTICE, THE CUNY



In the circuit shown above:

- Emf = a battery supplying 15 V.
- C = a capacitor of $30 \mu\text{F}$.
- R_1 = a resistor of 300Ω .
- R_2 = a resistor of 200Ω .
- R_3 = a resistor of 100Ω .

S_1 is a switch. Initially, it is CLOSED:
current can travel through the loop containing the switch.

S_2 is a switch. Initially, it is OPEN: current
CANNOT travel through the loop containing the switch.

Points A – F are just labeled locations in
the wire.

- a. Now the experiment begins: Assume that S_1 is CLOSED and S_2 is OPEN. It might help you to alter S_1 in the diagram.

Find I , the electric current, at each of the following locations.

A)

B)

C)

D)

E)

F)

- b. Continue to assume that S_1 is CLOSED and S_2 is OPEN. Also assume that the circuit is grounded at point F. That is, assume that $V = 0$ Volts at point F.

Find V , the electric potential, at each of the following points.

A)

B)


C)

D)

E)

NOW ASSUME that S_1 is OPEN and S_2 is CLOSED. It might help you to indicate this new reality on the diagram.

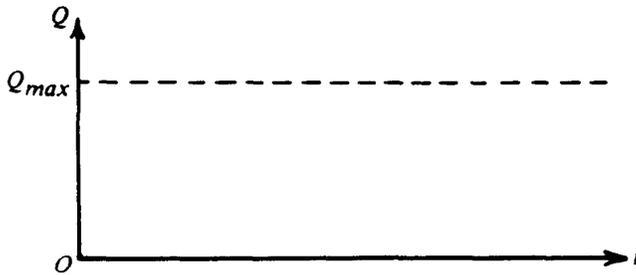- c. Using Energy conservation, Ohm's Law and the definition of capacitance, show the rate at which charge builds up in the capacitor as a function of time. That is, derive Q as a function of t —where \mathcal{E} , R_{123} and C are constants. R_{123} stands for the total, "equivalent" resistance provided by R_1 , R_2 and R_3 in this circuit.
- d. On your own copy of the axes below, neatly sketch the function you derived in (c), above. To the right of the axes, you **MUST INDICATE** the value of $Q(\text{max})$ in terms of \mathcal{E} , C and/or R_{123} (3 pts).



- e. In *seconds*, determine a **NUMERICAL VALUE** for the amount of time required for the current in this circuit to decay to $\frac{2}{3}$ of its original value.
That is: Determine t such that $I = \frac{2I_0}{3}$ (5 pts).